 


FPGA Stopwatch



Made by Vitaly Okolelov

Email: okolelovvitaly@gmail.com

GitHub: <https://github.com/okolelovv>

LinkedIn: <https://www.Linkedin.com/in/vitaly-okolelov-715699194/>


Functionality

Control signals:

- Start/stop: A falling edge starts the timer, next falling edge stops it
- Hold: Logic 0 pauses the timer; logic 1 enables it
- Reset: Logic 0 pulls the timer to 0 and keeps it there


Output:

 - Six 7-segment displays outputs minutes, seconds and tenths of seconds
- If the timer goes above its maximum range (99:59:99), the overflow LED is on



FPGA device

MAX 10 10M50DAF484C7G chip

 

Start/stop button

Hold button


Overflow LED

Reset switch

7-segment displays

DE-10 Lite Board

Modules and signals

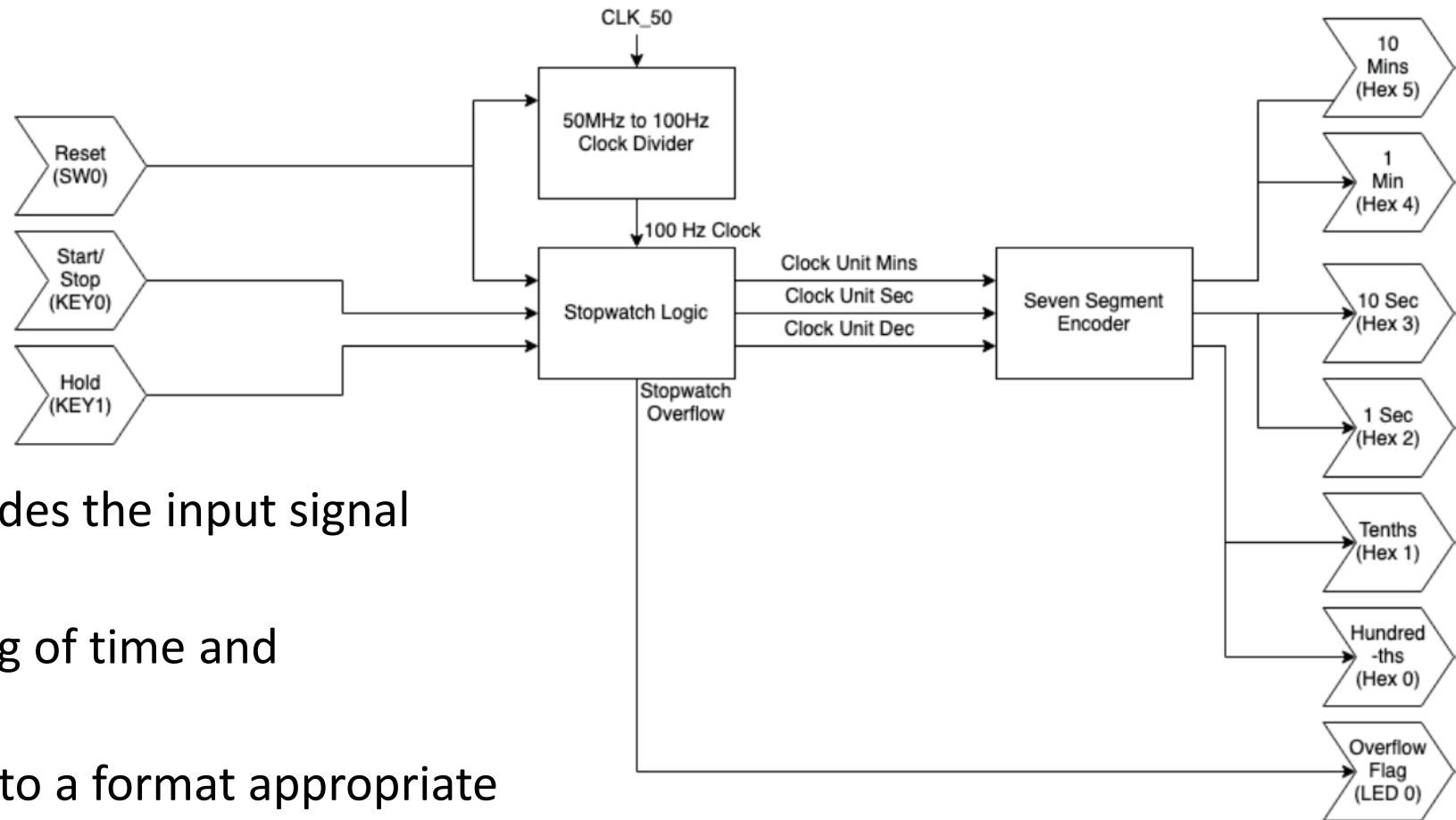

ClockDivider50MHzTo100Hz – divides the input signal frequency by 500,000

StopwatchLogic – handles counting of time and start/stop/reset functionality


SevenSegEncoder – converts time to a format appropriate for display on six seven-segment displays

Stopwatch – Top level design

Combination vs behavioural logic

When using behavioural logic, synthesis often results in having flip-flops in the design. The main type of flip-flops used in this project the RS-type flip-flop which is a D-type flip-flop that supports asynchronous set and reset.

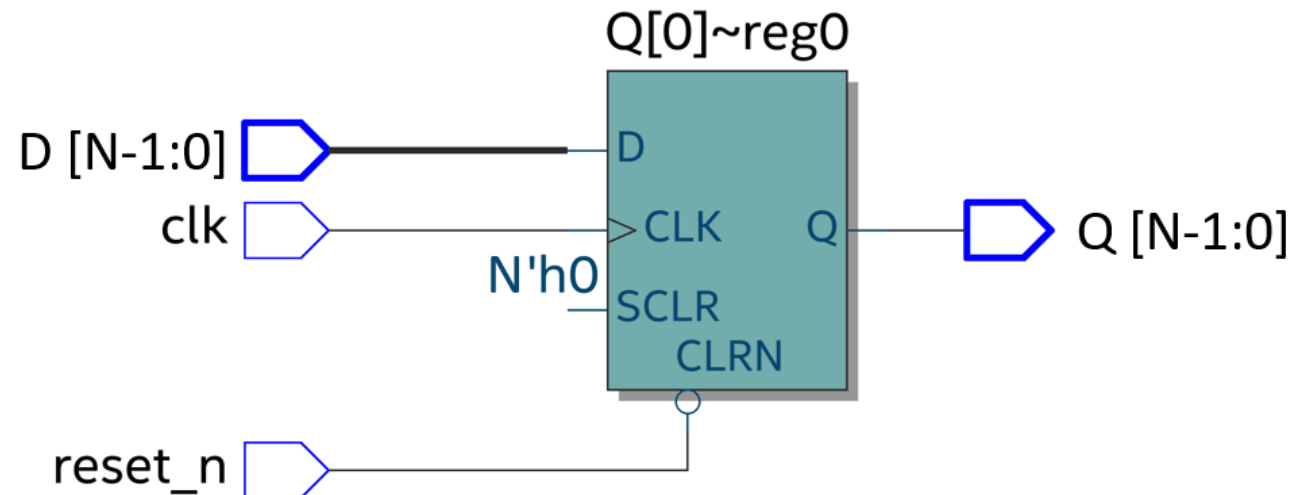Having this module allowed to significantly simplify the design and break it down into purely combinational logic.



Features of the Verilog code

To make module designs reusable, the following advanced (not yet studied at the university) techniques were used:

- Parameters
- Replication operator
- Generate blocks
- Tasks
- \$clog2 function

Design verification

- ModelSim was used for design verification
- Testbenches written in Verilog
- Different techniques used depending on situation:
 - Directed testing
 - Random testing
 - Constrained random testing


Results:

- Functional correctness was verified
- The accuracy of counting was confirmed down to nanoseconds

Pin mapping and programming the FPGA Device

Project was completed in Quartus software:

 - Pin Planner tool was used for pin assignment
- Then, the design was loaded on FPGA device and tested for correct behaviour



Thank you!